



① BASICS OF ELECTRIC NETWORK



The tutorial is useful to understand basics of electrical networks.

Resistor :-





l = length, a = Area of cross-section

$$R = \rho \frac{l}{a} \Omega$$

where ρ is resistivity in $\Omega\text{-m}$

Series circuit :-

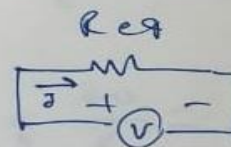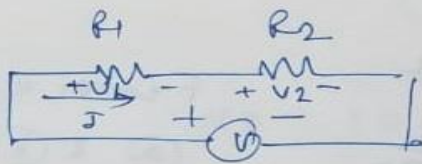Current through all elements remains same but voltage is divided. Voltage division rule is applicable to series circuit.



Apply KVL

$$V = V_1 + V_2$$

$$V = IR_1 + IR_2$$

$$\frac{V}{I} = R_1 + R_2 \quad \text{--- (1)}$$

$$V = I R_{eq} \quad \text{--- (2)}$$

From eq (1) & (2)

$$R_{eq} = R_1 + R_2 \Omega$$



Use voltage divider rule

$$V_1 = I R_1$$


$$V_1 = \frac{V}{R_1 + R_2} R_1$$

$$V_2 = I R_2$$

$$V_2 = \frac{V}{R_1 + R_2} R_2$$

Parallel circuit:

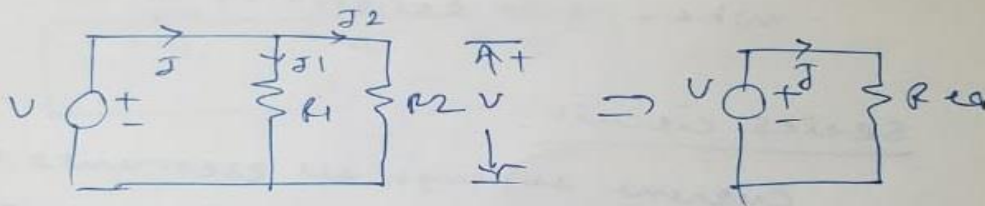current is divided & voltage across each element remains same. The current-division rule is applicable.



APPLY KCL

$$I = I_1 + I_2$$

$$= \frac{V}{R_1} + \frac{V}{R_2}$$

$$\frac{I}{V} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$G_{eq} = G_1 + G_2$$

$$G_1 = \text{conductance} = \frac{1}{R_1}$$

$$G_2 = \text{conductance} = \frac{1}{R_2}$$

$$V = I \left(\frac{R_1 R_2}{R_1 + R_2} \right) \text{ --- (a)}$$

$$V = I R_{eq} \text{ --- (b)}$$

From equation

(a) & (b)

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$



② Use current division rule for two resistors connected in parallel.




$$I_1 = \frac{V}{R_1} = \left(I \frac{R_2}{R_1 + R_2} \right) = I \frac{R_2}{R_1 + R_2} \text{ Amp}$$

$$I_2 = \frac{V}{R_2} = \left(I \frac{R_1}{R_1 + R_2} \right) = I \frac{R_1}{R_1 + R_2} \text{ Amp}$$

Exercise 5: Find V_1 , V_2 , V_3 for following

network

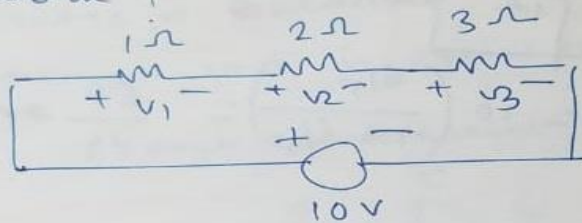

Apply voltage division rule


$$V_1 = 10 \left(\frac{1}{1+2+3} \right) = \frac{10}{6} \text{ volts}$$

$$V_2 = 10 \left(\frac{2}{1+2+3} \right) = \frac{20}{6} = \frac{10}{3} \text{ volts}$$

$$V_3 = 10 \left(\frac{3}{1+2+3} \right) = \frac{30}{6} = 5 \text{ volts}$$




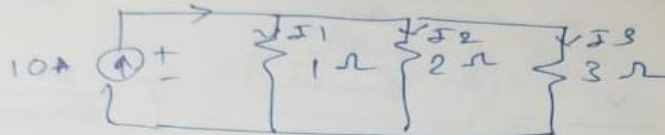Exercise II: Find I_1, I_2, I_3 for following circuit: $I = 10A$




Use current division rule

a)

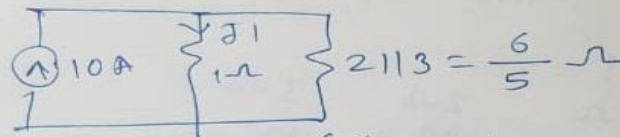


$$I_1 = 10 \left(\frac{6/5}{1 + 6/5} \right) = \frac{60}{11} \text{ Amp}$$

b)

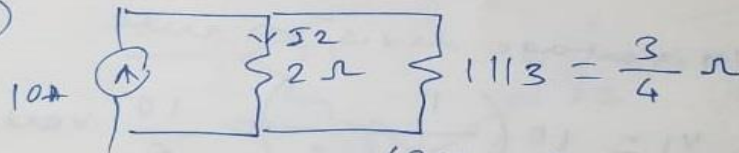

$$I_2 = 10 \left(\frac{3/4}{2 + 3/4} \right) = \frac{30}{11} \text{ Amp}$$

c)

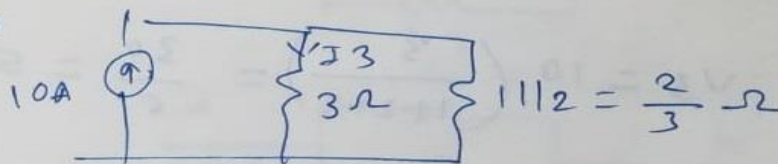

$$I_3 = 10 \left(\frac{2/3}{3 + 2/3} \right) = \frac{20}{11} \text{ Amp}$$

Note: current division rule is applicable to two resistors connected in parallel



Intelligent Freshers

Sample Tutorial


www.intelligentfreshers.com

(3)

→ Let us find the equivalent resistor seen from terminal a, b




a)


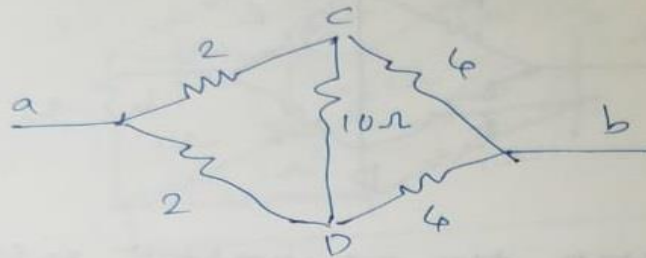


now as ratio of $\frac{2}{2} = \frac{4}{4}$ the bridge is balanced. Therefore current through 10Ω is equal to zero.

Sketch equivalent circuit-

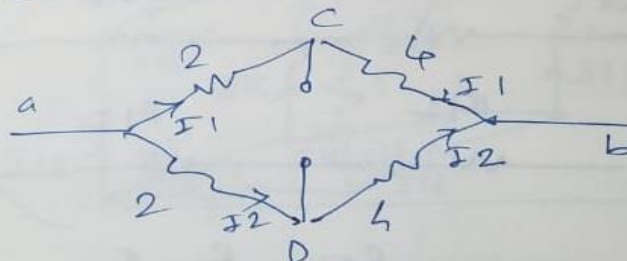

$$2 + 4 = 6$$

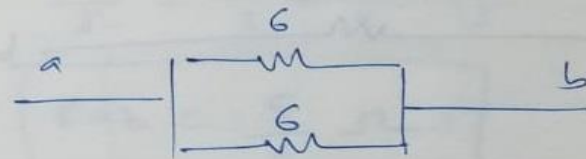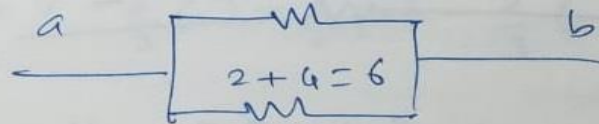

$$R_{ab} = 6 \parallel 6 = \frac{6 \times 6}{6 + 6} = 3\Omega$$

∴ $R_{ab} = 3\Omega$




Intelligent Freshers




Sample Tutorial

www.intelligentfreshers.com

b) Find R_{ab}

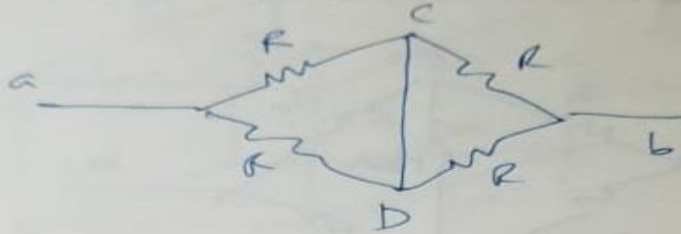

Sketch the equivalent circuit

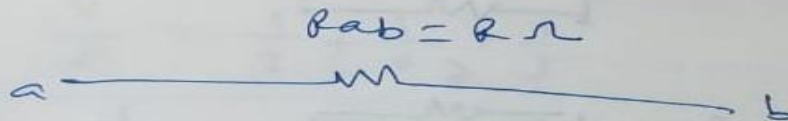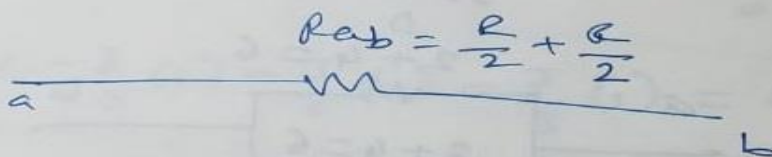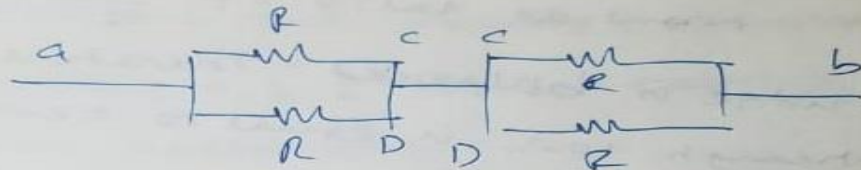



(4)

c) Find R_{ab}


→ Connect the voltage source of V across a, b & then from a to b path apply KVL

$$+V - \frac{I}{3}(1) - \frac{I}{2}(1) - \frac{I}{3}(1) = 0$$
$$\frac{V}{I} = \frac{1}{3} + \frac{1}{6} + \frac{1}{3}$$



$$R_{ab} = \frac{5}{6} \Omega$$




d) Find R_{ab}

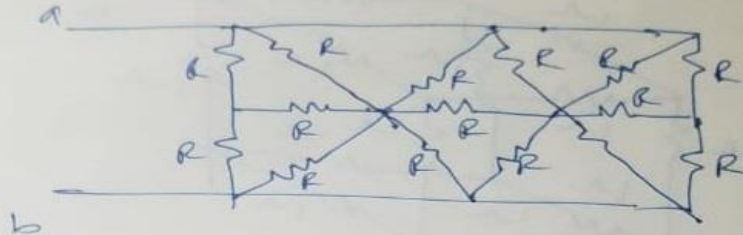

→ sketch the diagram

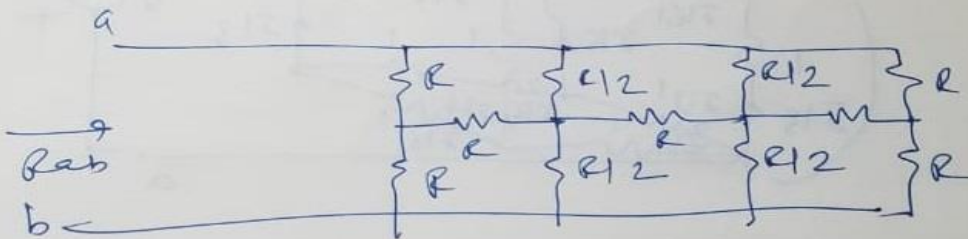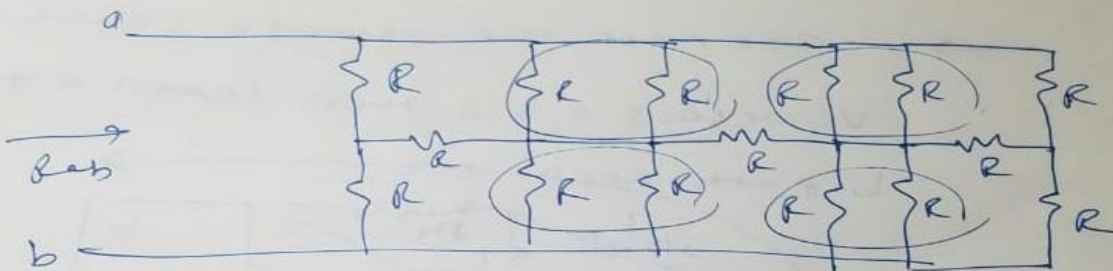

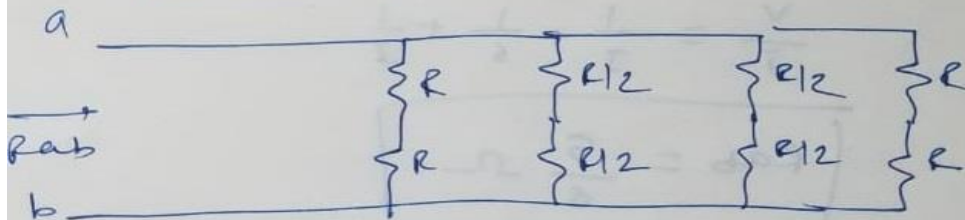From above network it is clear that we have balance bridge



$$\frac{1}{R_{ab}} = \frac{1}{2R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{2R} = \frac{3}{R}$$

$$R_{ab} = \frac{R}{3}$$